

Shift1 system for 1-wire shift registers

Using a shift register to get 7 or 8 output pins from 1 PIC pin! - 3rd Nov 2009.

What is it?

My **Shift1 System** is a cheap and simple way to get lots of digital output pins and only needs 1 PIC pin to drive it.

You can often buy CMOS Shift Register ICs very cheap, and this can be a great way to get more output pins from your PIC. But to drive a shift register generally needs 2 or 3 control pins... My system on this page only needs ONE PIC pin!


I should state that **I did not invent the idea of controlling a shift register with one RC network!** This is an old idea I have seen many years ago. What I wanted to do here was develop a system to work with LATCHED shift registers (ie I created a system that uses 2 RC networks and 3 shift register pins) and also I wanted to produce a ready-made workable system with C source code etc so people can easily make use of it.

How it works - the simple system

Normally, serial-in parallel-out shift register ICs can be set up for 2 pin operation;

- DAT - data, is the next bit to be shifted in
- CLK - clock pulse, on / edge the next bit is shifted in

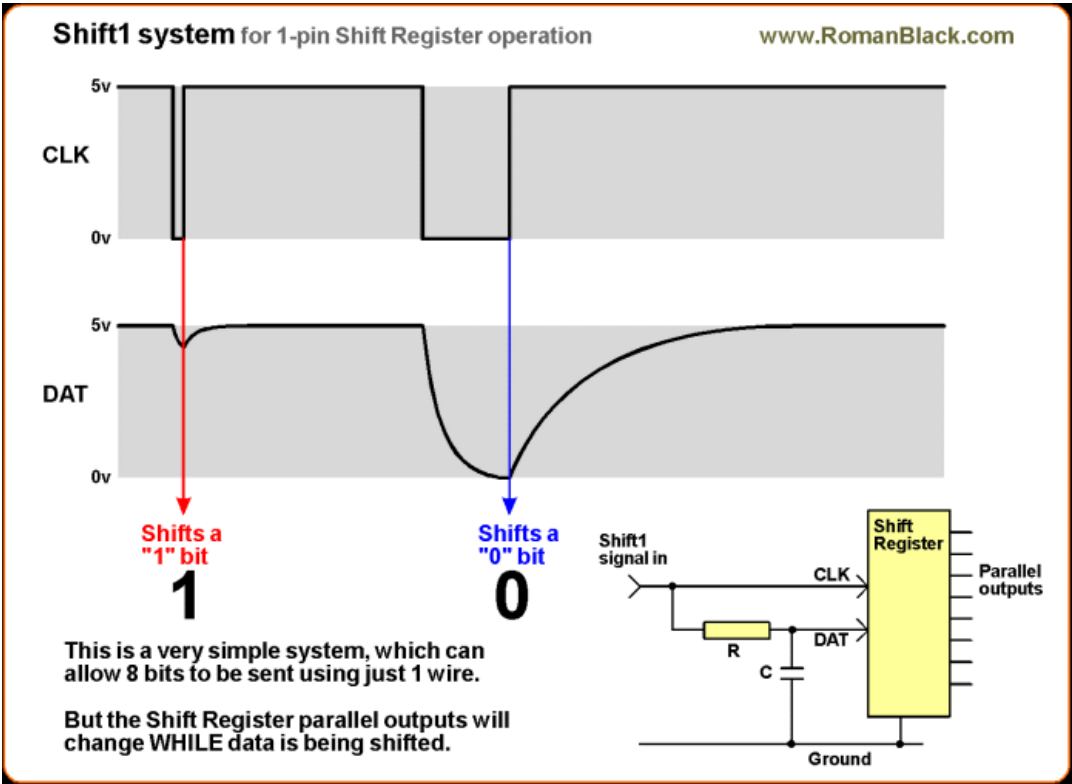This can be "cheated" to just use one pin and timed-length pulse. An RC network is used to provide a time delay for the DAT line to change. Very short pulses mean that a 1 bit is shifted in. With a long enough pulse the DAT voltage drops low enough so that a 0 bit is shifted in when the CLK line goes / again.




The system above works pretty good, all that is required is a Resistor and Capacitor, and then the pulse length determines if each new bit is shifted in as a 1 or 0.

The only drawback is that the data on the 8 parallel outputs changes as the new bits are shifted in. For many applications this doesn't matter, as it happens very quickly, generally less than a millisecond to shift all 8 bits in. So it can be used for things like LEDs, LED matrixing and keyboard matrixing etc.

Shift1 LATCHED system for driving LCDs

One of the things I wanted to use the Shift1 System for was driving a text LCD from 1 PIC pin. This is a very useful thing for me as I have lots of cheap shift register ICs and can then add a LCD to any PIC project that has ONE spare pin.

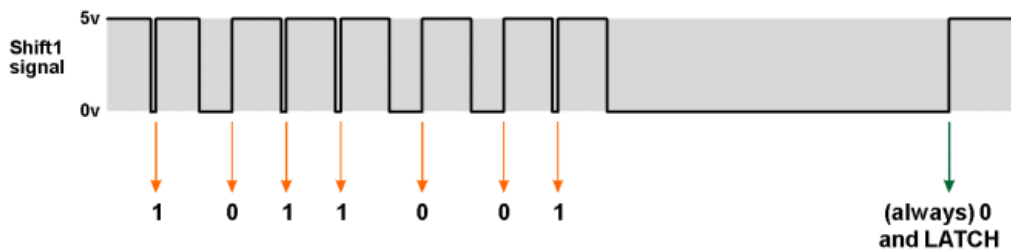
To drive a text LCD needs 6 pins; 4 data, RS and E. The E pin must be treated carefully so the basic Shift1 system shown above won't work. It needs a LATCHED system where the shift register's parallel outputs don't change until the register is "latched".



This system is very simple in hardware and allows Latched shift register output. So all bits are stable until the Latch command is received.

However the last bit (Bit0) is always zero.

So only 7 bits are available.

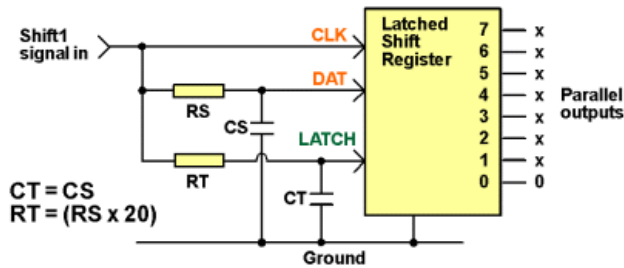


The Shift1 latched system is just an extension of the same concept. So 7 bits are sent first, then the 8th pulse is very long which triggers the latch event. I specifically designed this for the 74HC595 shift register IC which is common, cheap and has 20mA output drivers.

One obvious problem is that the last bit shifted in (bit0) will always be a zero. I though this was an acceptable tradeoff for such a neat system as to drive a text LCD only needs 6 bits, and it gives 7 bits.

A less obvious problem is that it is a little slow. Driving an LCD needs the latch data to be sent 4 times for each text character sent. Twice for the 4bit data, and twice to make the additional E pulses. This can take up to 4mS to send a character (usually around 3mS). It is fast enough for most display purposes and menus etc, unless you need to display a LOT of fast-changing numerical data.

Testing my Shift1 Latched protocol

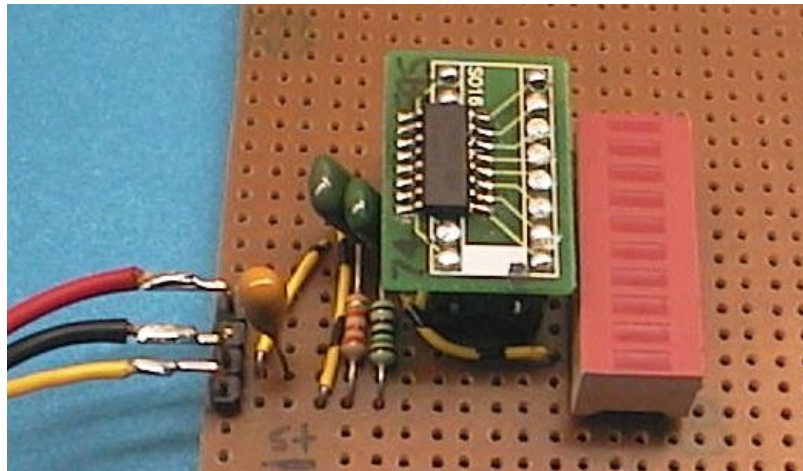


The "proof of concept" worked perfectly first go. I only had the 74HC595 in surface mount size, so I used a SO16 adapter board into a DIP16 socket.

The RC filter values are the same as shown in the schematic below;

1k5 2.2nF

33k 2.2nF

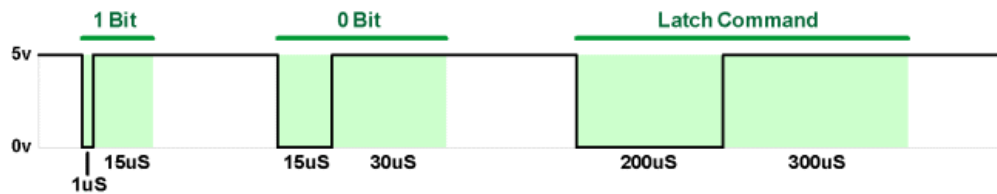Time periods to generate both types of Bit, and the final Latch Command;




Make 7 Bits - then the 8th Bit must be the Latch Command

These Resistor and Capacitor values have been tested with the uS timings shown above.

The timed periods in the green areas must be followed. The time between each Bit (white areas) does not matter.

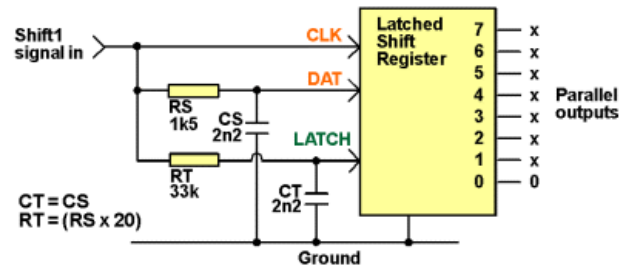When not making a Bit, the signal wire remains at 5V.




$$CT = CS$$

$$RT = (RS \times 20)$$

These values were chosen to give good comms speed, ie the shortest low pulse is 1uS which is a good value for PICs. The 1:20 ratio of the resistors was chosen to give a good safety margin between the low period needed to shift a low bit, and the low period needed to cause a latch command. I tested the shift register 8 output pins with a 8 bar LED. All 7 shift register pins worked perfectly, as expected.

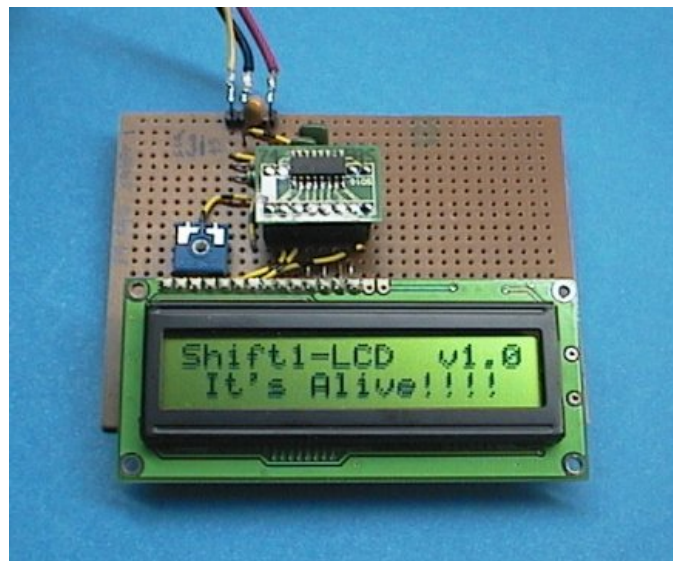I tested all the period times on the oscilloscope, and ended up with the uS periods shown in the diagram above. They have a safety margin built in, you may be able to use shorter periods.




The next test was to hook up a text LCD... I connected 6 of the 74HC595 pins to a typical LCD and added a 10k contrast pot. Then I adapted my C LCD code to write to the 6 pins through my Shift1 timed protocol. Everything worked fine, and was tested on a few different LCD displays. It's a success, one PIC pin driving a whole LCD and all that's needed is a shift register and a few discretes.


A practical Shift1 LCD driver

I designed a small PCB for using the Shift1 system to drive a text LCD. This only needs a 74HC595 shift register IC, 2 resistors and 2 caps, and a contrast trimpot to drive an LCD from 1 PIC pin.

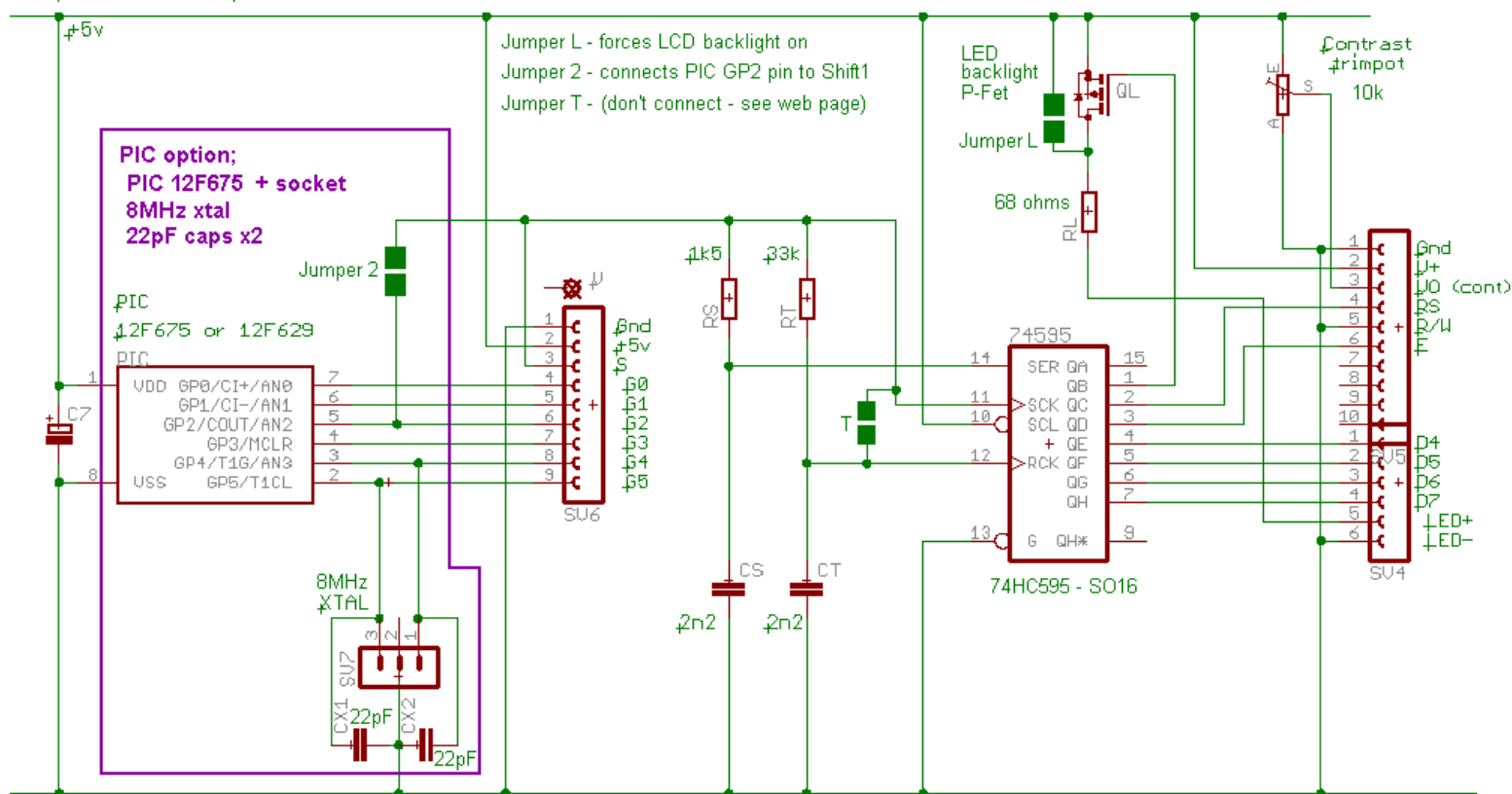The PCB mounts directly behind the LCD display, on the 16pin LCD header.



I also added space on the Shift1-LCD to include an optional 8pin PIC. As it only needs 1 pin to drive the LCD that still allows many simple applications with a little PIC. Another addition was a P-FET to control the LCD backlight (if it has one). This is done using the spare bit, so now all 7 outputs of the shift register are used and the PIC can turn the backlight on/off without needing any more pins.

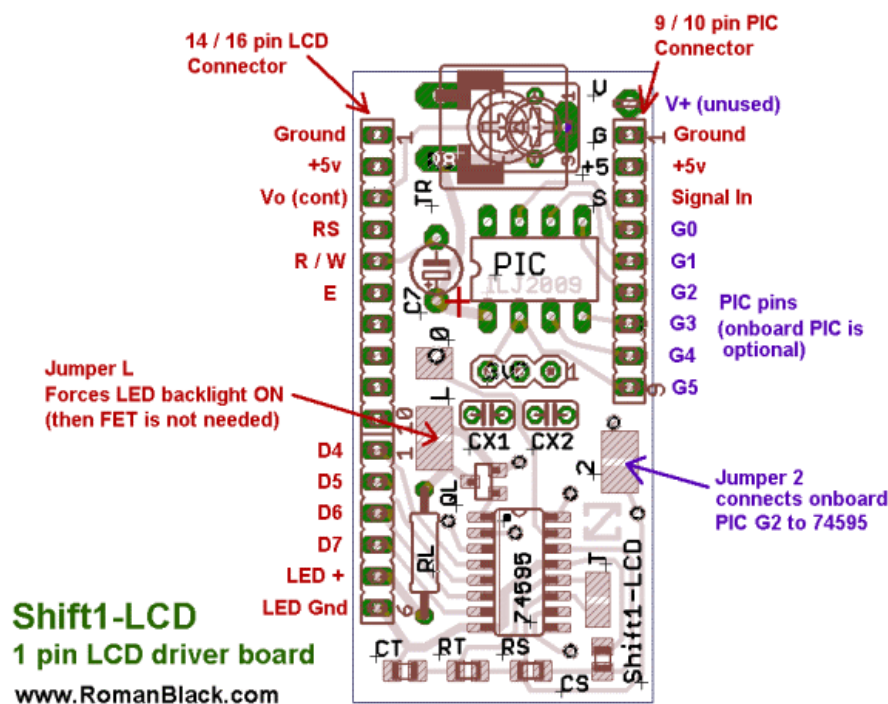

The Shift1-LCD module is available as a low cost kit in 2 forms;

- Standard; Kit without PIC microcontroller
- PIC Option; Kit also contains PIC 12F675, 8pin socket, 8MHz xtal and caps

Shift1-LCD with no PIC

Only needs 1 wire to control the whole LCD
- even the LED backlight

Signal 5v GND


This is the standard SHift1-LCD kit. As you can see above the Shift1 can be a complete LCD driver that only requires +5v, ground and ONE signal wire from any external PIC or other micro.

All Shift1-LCD kits now come with 16pin header and 16pin socket, so it can plug direct onto the back of your LCD. A 10pin angled header is also provided for the other connection.

Shift1-LCD www.RomanBlack.com

All the Shift1-LCD kits come with top quality PCBs and are very fast to assemble; about 15 minutes.


Shift1-LCD with PIC option!

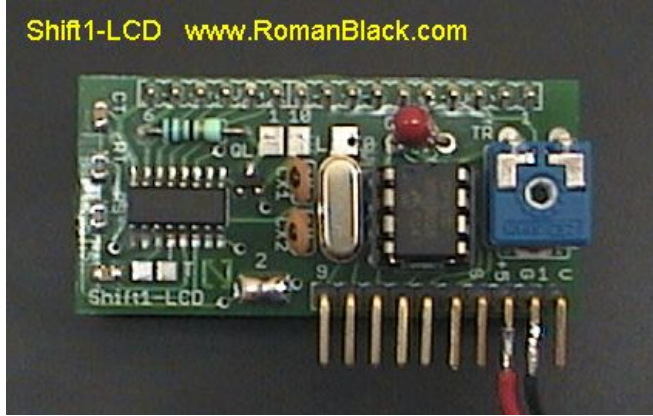

The **PIC Option** is an add-on kit for the Shift1-LCD that has a PIC 12F675 microcontroller (with 4 ADCs) a 8MHz xtal and caps (for precise timing tasks) and an 8pin socket for the PIC.

Now the Shift1-LCD can be a complete controller with LCD!

- Clocks - Timers - Counters
- Frequency and RPM display
- Thermometers and Temperature controllers
- Power supply controllers
- Solar battery charge controllers
- Chronographs
- Alarm controllers
- PWM controllers
- Message displays
- (the list goes on!)

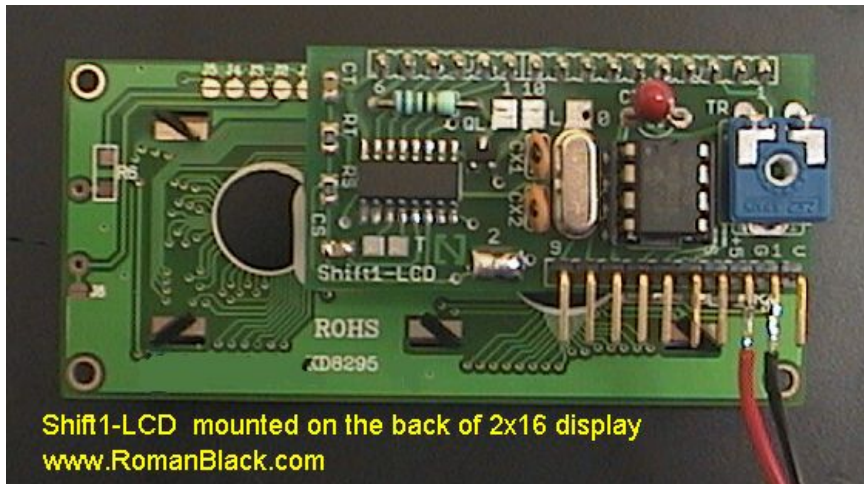

Shift1-LCD mounted on the back of 2x16 display
www.RomanBlack.com

- Shift1-LCD standard kit \$12 USD
 - Shift1-LCD with PIC option \$18 USD
- (You supply the LCD)

Buy Kits here! [Shift1-LCD Kits](#)

There are lots of Shift1-LCD [Projects Here!](#)

- end -

[\[Back to Home Page\]](#)